

EDTN Home Page

Search  
EDTNHit Enter to Search  
Advanced E-Search  
TM

News Center

Go to...

Design Center

Go to...

Career Center

Go to...

Network Partners


Go to...

EDTN Direct

Go to...

Interactive

Go to ...

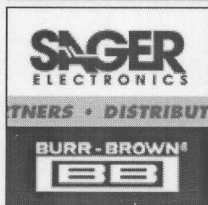Click Here for  
Advertising Info[feedback](#)

EDTN DESIGN CENTER

## ANALOG AVENUE

## Tech Notes

Download PDF

## Adding Dc Offset to an Amplifier

By Debbie Brandenburg,  
Applications Engineer, National Semiconductor

Are dc offset correction and gain accuracy concerns for you? There are several frequently used methods of adding dc offset to an amplifier and three methods will be compared and contrasted here:

1. Resistor using a non-inverting amplifier,
2. Resistor using an inverting amplifier,
3. Transistor using a non-inverting amplifier.

Two additional dc offset techniques will be noted.

The most common dc correction circuit uses a non-inverting amplifier and adds a dc voltage to the inverting terminal (see Fig. 1.)

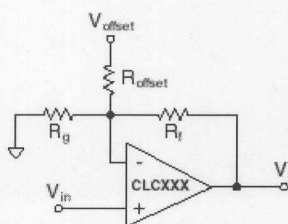


Figure 1: Dc Offset Method I: Non-inverting Configuration

The solution is simple and definitely adds a dc offset but this topology is not a simple solution if gain accuracy is also a major concern. The additional resistor,  $R_{offset}$ , is now a part of the gain equation. The transfer function of the circuit in Fig. 1 is:

$$V_o = V_{in} \left( 1 + \frac{R_f}{R_g} + \frac{R_f}{R_{offset}} \right) - \frac{V_{offset} R_f}{R_{offset}}$$

and the additional resistor,  $R_{offset}$ , must be considered when calculating the gain. Gain accuracy is now also dependent on the tolerance of 3 resistors instead of 2

What's new at Burr-Brown? A new Product Guide featuring the best price/performance products available. Order here!



Search EDTN and  
the Top 100  
Electronics Sites

Become a registered user of EDTN. Your free registration will make it easier for you to receive the information you need. See the [benefits of registration](#) or:

**Register Now**

[Privacy Statement](#)



An alternative solution is to simply change to an inverting configuration (see Fig. 2.)

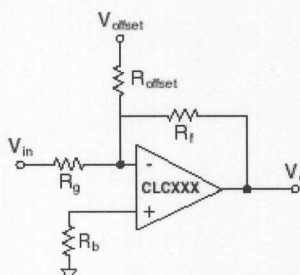


Figure 2: Dc Offset Method II: Inverting Configuration

This configuration provides a dc offset without affecting the gain; the transfer function for the circuit in Fig. 2 is:

$$V_o = -V_{in} \left( \frac{R_f}{R_g} \right) - \frac{V_{CC} R_f}{R_{offset}}$$

the additional resistor,  $R_{offset}$ , affects the amount of offset added to the amplifier, not the original gain. If a simple  $180^\circ$  phase shift is tolerable in the design, then use this method of adding dc offset. The lack of effect on gain is not the only advantage to operating in an inverting configuration, in most cases amplifiers operate faster in an inverting configuration and you reduce the chances of saturating the input.

A third method of adding dc offset to an amplifier (illustrated in Fig. 3) uses a non-inverting amplifier and a transistor to add offset to the inverting node:

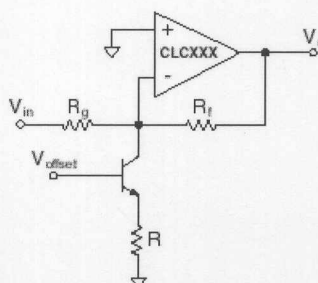


Figure 3: Dc Offset Method III: Inverting Configuration with Transistor

This third method uses a transistor to add current into the inverting node. The transistor's collector is a high impedance and, to a first measure, does not affect the amplifier's loop gain. The resulting transfer function is:

$$V_o = -V_{in} \left( \frac{R_f}{R_g} \right) + \frac{R_f (V_{offset} - 0.7)}{R}$$

Two additional methods (3 and 4) are also commonly used techniques of adding offset to an amplifier. Method 3 employs a non-inverting amplifier and a resistor that adds offset to the non-inverting terminal. Fig. 4 illustrates this technique:

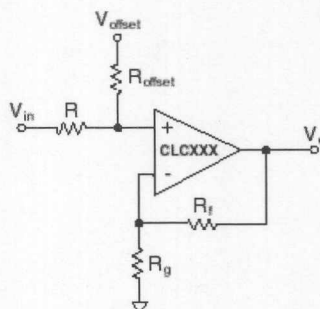


Figure 4: Dc Offset Method IV

$$V_o = \left( \frac{V_{in}}{1 + \frac{R}{R_{offset}}} \right) \left( 1 + \frac{R_f}{R_g} \right) + \left( \frac{V_{offset}}{1 + \frac{R_{offset}}{R}} \right) \left( 1 + \frac{R_f}{R_g} \right)$$

Method 5 uses an inverting amplifier and a resistor that adds offset to the non-inverting terminal and Fig. 5 shows this technique:

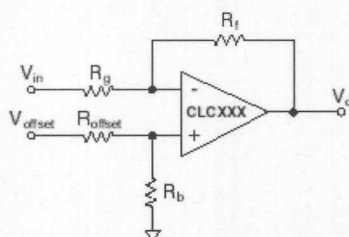


Figure 5: Dc Offset Method V

$$V_o = -V_{in} \frac{R_f}{R_g} + \frac{V_{offset} R_b}{R_g} \left( \frac{R_f + R_g}{R_b + R_{offset}} \right)$$

[Home](#) | [Product of the Week](#) | [Columns](#) | [Editorial](#) | [Tech Notes](#) | [Calendar](#)  
[Technology Diary](#) | [Manufacturers' Forum](#)



All material on this site Copyright © 1999 CMP Media Inc. All rights reserved.